

Unit II — Combinational Logic: MSI Devices

- Combinational Logic: output depends ONLY on current inputs — no memory or feedback
- MSI (Medium Scale Integration): ICs containing 12–100 gates on one chip
- Key devices covered: Comparator, MUX, DEMUX, Decoder, Encoder, Adders, Subtractors


"In combinational circuits, the same input always produces the same output — instantly, with no stored state."

1. Magnitude Comparator

- Compares two binary numbers A and B → gives three outputs: $A > B$, $A = B$, $A < B$
- Works bit-by-bit from MSB to LSB; first differing bit decides the result

1-bit Comparator — Boolean Equations

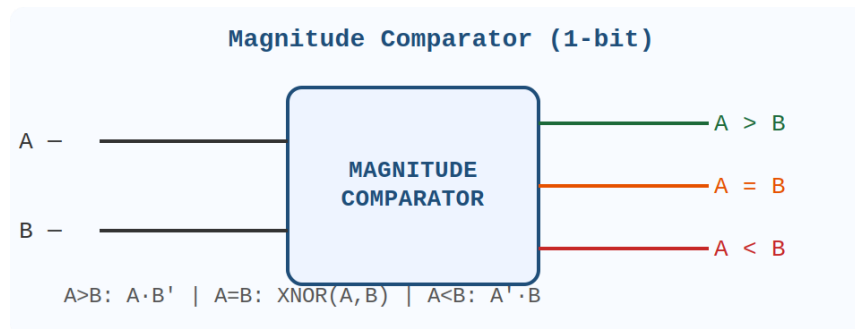- $A > B \rightarrow A \cdot B'$
- $A = B \rightarrow A \text{ XNOR } B = A'B' + AB$
- $A < B \rightarrow A' \cdot B$



4-bit Comparator — IC 7485

- Compares two 4-bit numbers; evaluates pairs from bit 3 (MSB) down to bit 0 (LSB)
- Has cascading inputs ($IA > B$, $IA = B$, $IA < B$) — connect outputs of lower chip to inputs of higher chip
- Chain two IC 7485 chips → 8-bit comparison; four chips → 16-bit comparison

🔗 Example: Compare $A = 1011$ (11) and $B = 1001$ (9) → $A > B$ output = HIGH


A	B	A > B	A = B	A < B
0	0	0	1	0
0	1	0	0	1
1	0	1	0	0
1	1	0	1	0

2. Multiplexer (MUX)

- MUX = Many-to-One selector: picks ONE of N inputs and routes it to a single output
- A 2^n -to-1 MUX requires exactly n select lines

Boolean Expressions

 - 2-to-1 MUX : $Y = S' \cdot I_0 + S \cdot I_1$
- 4-to-1 MUX : $Y = S_1'S_0' \cdot I_0 + S_1'S_0 \cdot I_1 + S_1S_0' \cdot I_2 + S_1S_0 \cdot I_3$



Common ICs

- IC 74151 → 8-to-1 MUX (3 select lines)
- IC 74153 → Dual 4-to-1 MUX (2 select lines each)

Applications

- Data routing between multiple sources and one destination
- Parallel-to-serial data conversion
- Implementing any Boolean function (universal logic element)

🔗 Example: 4-to-1 MUX with $S_1=0, S_0=1$ → selects I_1 as output, regardless of I_0, I_2, I_3


💡 A 2^n -to-1 MUX can implement ANY Boolean function of n variables — just connect minterms to inputs.

3. Demultiplexer (DEMUX)

- DEMUX = One-to-Many distributor: routes ONE input signal to ONE of N output lines
- Exact inverse operation of a MUX
- 1-to-4 DEMUX → 2 select lines; 1-to-8 DEMUX → 3 select lines

Output Equation

 - $Y_i = D_{in} \cdot (\text{select combination for output } i)$
- Only the selected output follows D_{in} ; all others remain 0



Common ICs

- IC 74139 → Dual 1-to-4 DEMUX
- IC 74138 → 1-to-8 DEMUX (also functions as a 3-to-8 decoder)

Applications

- Data distribution from one source to multiple destinations
- Serial-to-parallel data conversion
- Memory address decoding alongside decoders

🔗 Example: 1-to-4 DEMUX, $D_{in} = 1$, $S1 = 0$, $S0 = 1 \rightarrow Y1 = 1$, $Y0 = Y2 = Y3 = 0$


4. Decoder

- Converts an n-bit binary input into one of 2^n unique output lines (n-to- 2^n)
- Exactly ONE output is HIGH at any time (active-high) — or LOW (active-low decoder)
- Optional Enable (EN) pin: when $EN = 0$, all outputs are disabled (= 0)

2-to-4 Decoder — Output Equations

- $D0 = A1' \cdot A0'$ (input = 00)
- $D1 = A1' \cdot A0$ (input = 01)

 - $D2 = A1 \cdot A0'$ (input = 10)
- $D3 = A1 \cdot A0$ (input = 11)



Common ICs

- IC 74138 → 3-to-8 decoder (most exam-relevant; has 3 enable pins)
- IC 7442 → BCD-to-Decimal (4-to-10) decoder
- IC 7447 → BCD-to-7-segment decoder (drives 7-segment displays directly)

Applications

- Memory chip-select logic — activate one memory bank at a time
- CPU instruction decoding — identify which operation to execute
- Seven-segment display driving via BCD decoder (IC 7447)

✂ Example: 3-to-8 decoder, input $A2A1A0 = 101$ → only $D5 = \text{HIGH}$, $D0$ – $D4$ and $D6$ – $D7 = \text{LOW}$

💡 Decoder can implement any combinational function — OR the required minterm outputs together.

5. Encoder


- Inverse of a decoder: converts 2^n one-hot inputs into an n -bit binary output code
- Standard encoder limitation: only ONE input must be active at a time

4-to-2 Encoder — Output Equations

- $A1 = I2 + I3$
- $A0 = I1 + I3$

Priority Encoder

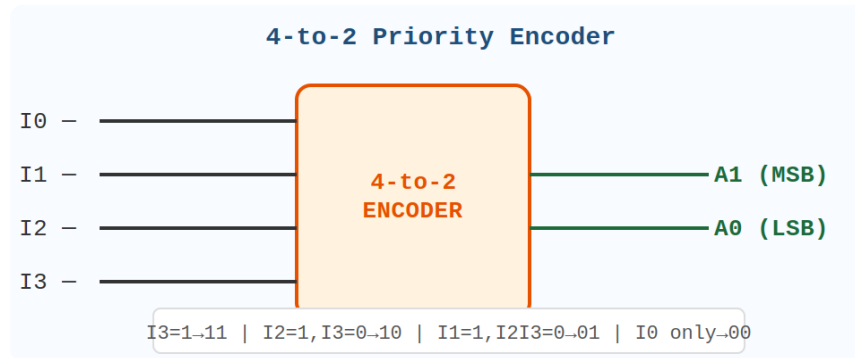- Solves the multiple-active-input problem — the highest-indexed active input wins
 - 4-to-2 Priority Encoder: $A1 = I3 + I2$ $A0 = I3 + I1 \cdot I2'$
 - Has a Valid Output (V) flag: $V = 1$ when at least one input is active



Common ICs

- IC 74147 → 10-to-4 BCD priority encoder (decimal keypad → BCD)
- IC 74148 → 8-to-3 octal priority encoder

Applications

- Keyboard encoding — each key press produces a binary code
- Interrupt priority controllers — highest-priority interrupt gets CPU
- Data compression — encode active lines to fewer bits


- ✂ Example: 4-to-2 priority encoder: I3 = 1 (highest priority active) → output A1A0 = 11 (regardless of I0, I1, I2)
- ✂ Example: Keyboard encoder: pressing '7' on a decimal keypad → IC 74147 outputs BCD 0111

6. Multiplexed Display

 - Problem: driving N seven-segment displays statically needs $N \times 7$ segment wires — too many
- Solution: share one set of 7 segment lines; rapidly scan which digit is active

How It Works — Step by Step

- Step 1: Controller outputs BCD data for Digit 0 on the shared 7-segment bus
- Step 2: Digit 0 common pin is enabled (anode pulled HIGH / cathode pulled LOW)
- Step 3: After ~1 ms, Digit 0 is disabled; data for Digit 1 is placed on the bus
- Step 4: Digit 1 is enabled for ~1 ms; then cycle moves to Digit 2, Digit 3, ...
- Step 5: The full scan repeats at ≥ 1 kHz — persistence of vision makes all digits appear lit



Key Facts

- Refresh rate must exceed 50 Hz per digit to avoid visible flicker
- N digits require only $7 + N$ control lines (vs $7 \times N$ for static driving)
- IC 7447 (BCD-to-7-segment decoder) is used together with digit-select transistors

✂ Example: 4-digit clock display: scan cycle = 4 ms total; each digit ON for ~1 ms per cycle


💡 Multiplexed display is Time-Division Multiplexing (TDM) applied to LEDs — same principle as TDM in communications.

7. Half Adder

- Adds two 1-bit numbers A and B; produces Sum (S) and Carry-out (C)
- Cannot accept a carry-in from a previous stage — limited to first bit position

Boolean Equations

 - $S = A \oplus B$ (implemented with XOR gate)
- $C = A \cdot B$ (implemented with AND gate)




✂ Example: $A = 1, B = 1 \rightarrow S = 0, C = 1$ (binary: $1 + 1 = 10$)

8. Full Adder

- Adds three 1-bit inputs: A, B, and Carry-in (C_{in}) from the previous stage
- Built using two Half Adders and one OR gate

Boolean Equations

 - Sum $S = A \oplus B \oplus \text{Cin}$
- Carry $\text{Cout} = A \cdot B + \text{Cin} \cdot (A \oplus B)$ [equivalently: $AB + B\text{Cin} + A\text{Cin}$]



A	B	Cin	Sum (S)	Cout
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

9. Half Subtractor

- Subtracts B from A (both 1-bit); produces Difference (D) and Borrow-out (Bout)

Boolean Equations

- $D = A \oplus B$
- $\text{Bout} = A' \cdot B$ (borrow occurs when $A = 0$ and $B = 1$)

🔗 Example: $A = 0, B = 1 \rightarrow D = 1, \text{Bout} = 1$ (0 – 1 requires borrowing)

10. Full Subtractor

- Computes $A - B - \text{Bin}$ (includes Borrow-in from the previous stage)
- Built using two Half Subtractors and one OR gate — mirror of Full Adder structure

Boolean Equations

- $D = A \oplus B \oplus \text{Bin}$
- $\text{Bout} = A' \cdot B + A' \cdot \text{Bin} + B \cdot \text{Bin}$

🔗 Example: $A = 1, B = 1, \text{Bin} = 1 \rightarrow D = 1, \text{Bout} = 1$

Feature	Half Subtractor	Full Subtractor
Inputs	2 (A, B)	3 (A, B, Borrow-in)
Outputs	Difference, Borrow-out	Difference, Borrow-out
Difference eqn	$A \oplus B$	$A \oplus B \oplus \text{Bin}$
Chainable?	No (no Borrow-in)	Yes (cascades stages)

11. Serial Adder

- Adds two n-bit numbers one bit per clock cycle, starting from the LSB

Components


- 1 Full Adder (does the actual addition each cycle)
- 2 Shift Registers (hold operands A and B, shift right each cycle)
- 1 D Flip-Flop (stores Carry-out; becomes Carry-in for the next cycle)

Operation — Step by Step

- Step 1: Load n-bit numbers A and B into shift registers (LSB at output end)
 - Step 2: Clock pulse $\rightarrow$ LSBs of A and B shift into Full Adder inputs
 - Step 3: FA computes Sum bit; stored in result register, and Cout stored in D flip-flop
 - Step 4: Next clock $\rightarrow$ next bits shift in; D flip-flop output is Cin for this cycle
 - Step 5: Repeat for all n bits $\rightarrow$ n clock cycles total
- Advantage: only 1 Full Adder needed regardless of word length — minimal hardware
 - Disadvantage: n clock cycles to complete — very slow for large operands

 12. Parallel (Ripple Carry) Adder

- Adds all n bits of A and B simultaneously using n Full Adders connected in cascade
- Carry-out of each FA becomes the Carry-in of the next — carry 'ripples' left to right



- IC 7483: standard 4-bit parallel binary adder — most common in labs and exams
- Worst-case delay = $n \times (\text{single FA carry propagation delay})$ — slow for large n
- Solution for speed: Carry Look-Ahead Adder (CLA) — computes all carries simultaneously

✂ Example: 4-bit adder: $A = 1010$ (10) + $B = 0110$ (6) → Sum = 10000, Cout = 1 (decimal 16 ✓)

Feature	Serial Adder	Parallel (Ripple) Adder
Speed	Slow (n clock cycles)	Faster (1 cycle + ripple delay)
Hardware	1 FA + 2 shift regs + 1 DFF	n Full Adders
Carry handling	D flip-flop (clocked)	Ripples from $FA_0 \rightarrow FA_{n-1}$
Cost	Low (minimal gates)	Higher (scales with n)
Use case	Area-constrained, low speed	General-purpose digital systems

13. BCD Adder

- Adds two BCD (Binary Coded Decimal) digits, each representing 0–9
- Problem: raw binary addition can produce results 10–15 (binary 1010–1111) — invalid BCD codes

Correction Rule

- If Sum > 9 OR Carry-out = 1 → add correction factor 0110 (6) to the result
- Correction detect: $C4 + S3 \cdot S2 + S3 \cdot S1$ ($C4$ = carry-out, $S3$ – $S0$ = sum bits)
- After correction, a carry-out of 1 is generated and passed to the next BCD stage

✂ Example: 7 (0111) + 6 (0110) = binary 1101 (13 — invalid BCD) → add 0110 → 0001 0011 = BCD 13 ✓

✂ Example: 5 (0101) + 4 (0100) = binary 1001 (9) — valid BCD, no correction needed ✓

Binary Sum Result	Decimal Equivalent	Valid BCD?	Action Required
0000 – 1001	0 – 9	Yes ✓	No correction — output directly
1010 – 1111	10 – 15	No ✗	Add 0110 (6); generate carry-out = 1
Carry-out = 1	16 +	No ✗	Add 0110 (6); carry propagates to next stage

Quick Comparison — All MSI Devices

Device	Function	I/O Summary	Key IC
Magnitude Comparator	Compare two binary numbers	$2 \times n\text{-bit} \rightarrow 3$ flag outputs	IC 7485
Multiplexer (MUX)	Select 1 of N inputs $\rightarrow$ 1 output	2^n inputs + n sel $\rightarrow$ 1	IC 74151, 74153
Demultiplexer (DEMUX)	Route 1 input $\rightarrow$ 1 of N outputs	1 input + n sel $\rightarrow 2^n$	IC 74138, 74139
Decoder	Binary $\rightarrow$ one-hot output	n inputs $\rightarrow 2^n$ outputs	IC 74138, 7442
Encoder	One-hot $\rightarrow$ binary code	2^n inputs $\rightarrow$ n outputs	IC 74147, 74148
Half Adder	Add 2 bits	A, B $\rightarrow$ S, C	Discrete gates
Full Adder	Add 3 bits (with Cin)	A, B, Cin $\rightarrow$ S, Cout	IC 7483
Half Subtractor	Subtract 2 bits	A, B $\rightarrow$ D, Bout	Discrete gates
Full Subtractor	Subtract with Borrow-in	A, B, Bin $\rightarrow$ D, Bout	Discrete gates
Serial Adder	Add n-bit, 1 bit/cycle	Shift regs + 1 FA	Custom
Parallel Adder	Add n-bit simultaneously	n FAs in cascade	IC 7483
BCD Adder	Add BCD digits (0–9)	Parallel adder + correction	IC 7483 + logic

Glossary

Term	Definition
Combinational Logic	Digital circuit where output depends only on present inputs — no memory
MSI	Medium Scale Integration — ICs with 12–100 logic gates on one chip
MUX	Multiplexer — selects one of several inputs and routes it to a single output
DEMUX	Demultiplexer — routes one input to one of several outputs via select lines
Decoder	Converts n-bit binary input to one-of- 2^n active output (only one HIGH at a time)
Encoder	Converts one-of- 2^n active input to n-bit binary output code
Priority Encoder	Encoder where the highest-indexed active input takes output priority
Magnitude Comparator	Compares two binary numbers; outputs $A > B$, $A = B$, or $A < B$
Half Adder	Adds two 1-bit numbers; outputs Sum and Carry (no carry-in accepted)
Full Adder	Adds three 1-bit values (A, B, Cin); outputs Sum and Carry-out
Ripple Carry Adder	Parallel adder where carry propagates (ripples) from LSB to MSB stage
Serial Adder	Adds n-bit operands one bit per clock using shift registers and one FA
BCD	Binary Coded Decimal — each decimal digit 0–9 encoded as 4 binary bits
BCD Adder	Adds BCD digits; adds correction factor 6 (0110) when result exceeds 9
7-Segment Display	Display with 7 LED segments (a–g) arranged to show decimal digits 0–9
Multiplexed Display	Scanning display technique — digits enabled one at a time rapidly; uses fewer wires
Persistence of Vision	Human eye retains image ~20 ms; makes rapidly scanned digits appear continuously lit

Term	Definition
Carry Propagation Delay	Time for carry to ripple through all FA stages in a parallel adder
Enable (EN) Pin	Control pin on decoder/DEMUX; when inactive, all outputs are disabled
Cascading	Connecting multiple IC chips to extend bit-width (e.g., two 7485 → 8-bit compare)

END OF NOTES



ZenYukti

Quick Exam Notes

zenyukti.in



Other Unit Notes

All subject notes on GitHub — free to access & star

github.com/ZenYukti/MyNotes



Join ZenYukti Discord

Free workspace — internship & hackathon updates, tech discussions

go.zenyukti.in/discord

FIND US ON



Made with care by **ZenYukti** · Share freely, learn together

[Quick Exam Notes](#)

[Exam Ready](#)

[Free Resource](#)